

University of Bahrain
College of Information technology
Department of Computer Engineering

Test (1)

Student Name	
I.D. No.	
Section	

Course Title: Digital Logic
Course number: ITCE 202
Semester: 1
Academic Year: 2009/2010
Duration : 1hour
Date: 15th November 2009

Read the following before you start:

1. Write your name, ID and section number
2. Answer all questions.
3. Write your answers on the attached sheets only.

Question	Mark	Mark attained
1	15	
2	15	
3	15	
4	5	
Total	50	

Question [1]: [15 mark]

(a) Convert the following numbers showing all steps.

[2 marks each]

$$(110)_{10} = (\quad)_2$$

$$(673.2)_8 = (\quad)_{16}$$

$$(5)_{10} = (\quad)_{7-3-2-2}$$

$$(+17)_{10} = (\quad)_{1\text{'s complement}}$$

$$(-32)_{10} = (\quad)_{2\text{'s complement}}$$

$$(33)_4 = (\quad)_{10}$$

(b) Add the following numbers in BCD


[3 marks]

$$(48)_{10} + (52)_{10} =$$



Question [2] : [15 marks]

For the circuit shown below:

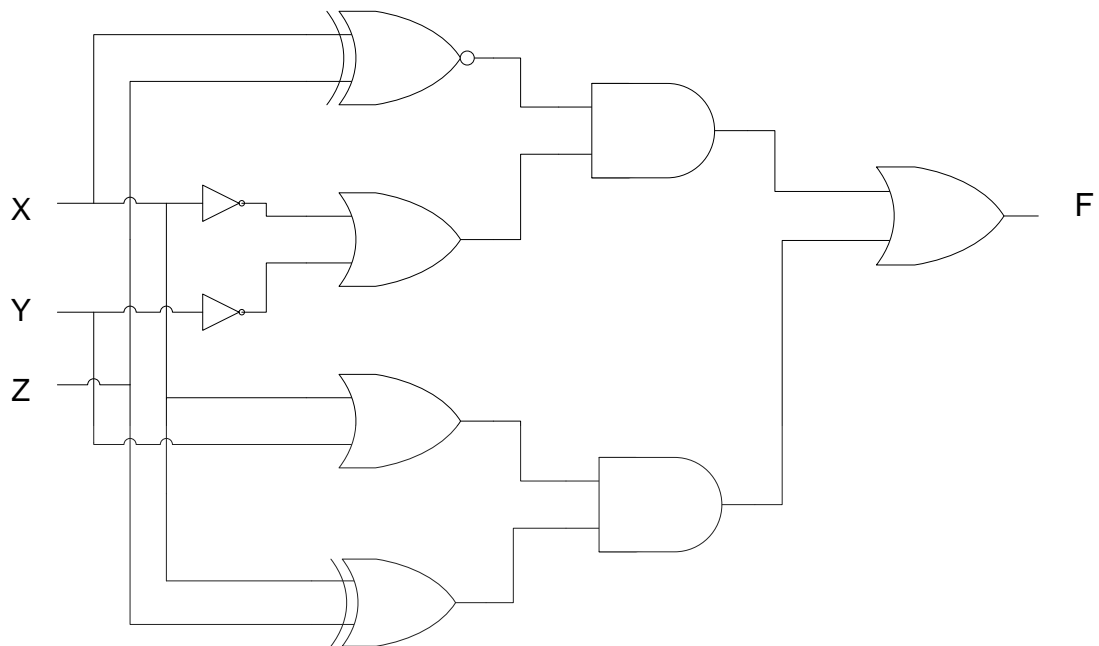

(a) Find the output expression F

(b) Prove algebraically that the resultant output expression is equal to:

$$F = (X \oplus Y) + \bar{Z}$$



(c) Express the following in SOP form (apply DeMorgan's Law, do not simplify):

$$F = [(A + CD)BD' + C \oplus D]'$$



Question [3]:**[15 marks]**

A combinational circuit is divided into two sub-circuits N1 and N2. The input of N1 is a 4bit binary number ABCD, where A is the MSB. The output of N1 is a binary number, XYZ with X being the MSB, whose value equals the number of 1's at the input. The output of N2 represents an excess-3 coded number, MNOP with M being the MSB, whose value equals the binary number received from N1.

- a. Determine the truth table for each sub-circuit separately, indicating all don't care conditions.
- b. Find the minterm expansion of the output M.
- c. Find the Maxterm expansion of the output O
- d. Draw the simplest logic circuit for the sub-circuit N2



Question [4]: [5 mark]

Given $F = A B' C' + A' B' D + A' C D + B C D$

- a) Use a K-map to find the minimum Product of Sums for F.
- b) Indicate the essential Prime Implicants in your answer and tell why each one is essential underling the minterm.

